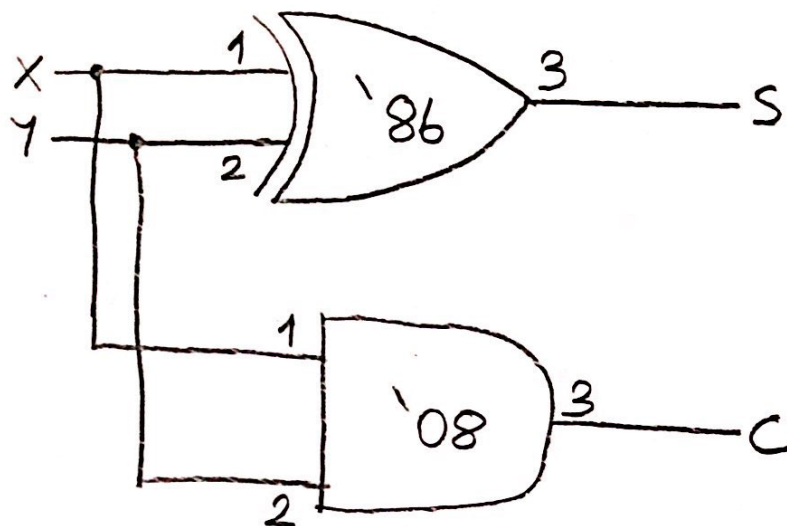


# - Half Adder -

Esad ismail Tok  
21801679



## IC List

One 7486 Quad 2-Input XOR Gate

One 7408 Quad 2-Input AND Gate

7486

GND-7


Vcc-14

7408

GND-7

Vcc-14

# - Half Subtractor -

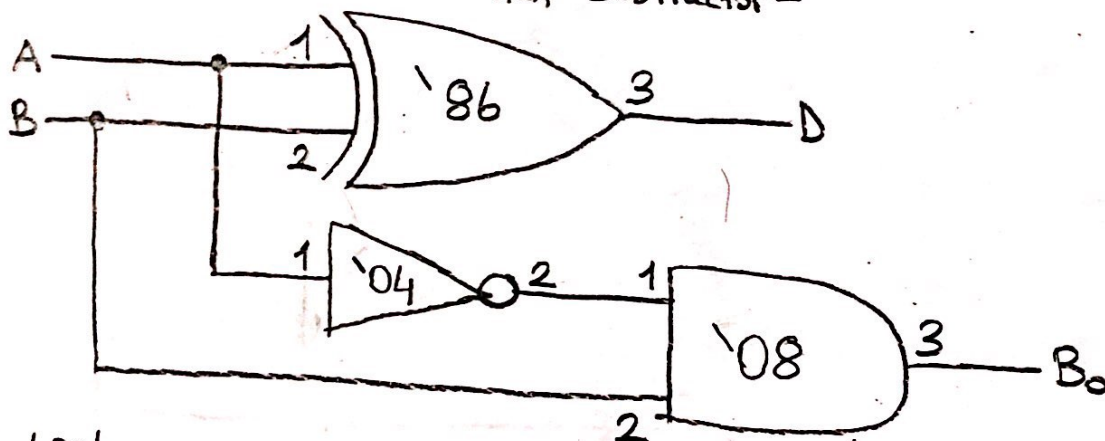

## IC List

One 7486 Quad 2-Input XOR Gate

One 7408 Quad 2-Input AND Gate

One 7404 Six Inverter

7486

GND-7

Vcc-14

7408

GND-7


Vcc-14

7404

GND-7

Vcc-14

# - Lab Calculator -

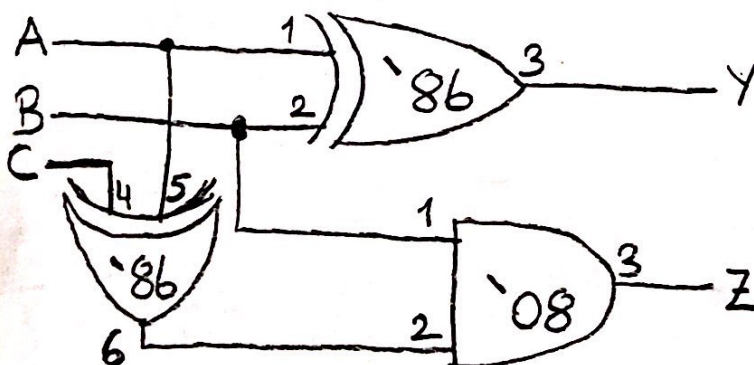

## IC List

One 7486 Quad 2-Input XOR Gate

One 7408 Quad 2-Input AND Gate

7408

GND-7

Vcc-14

7486

GND-7

Vcc-14