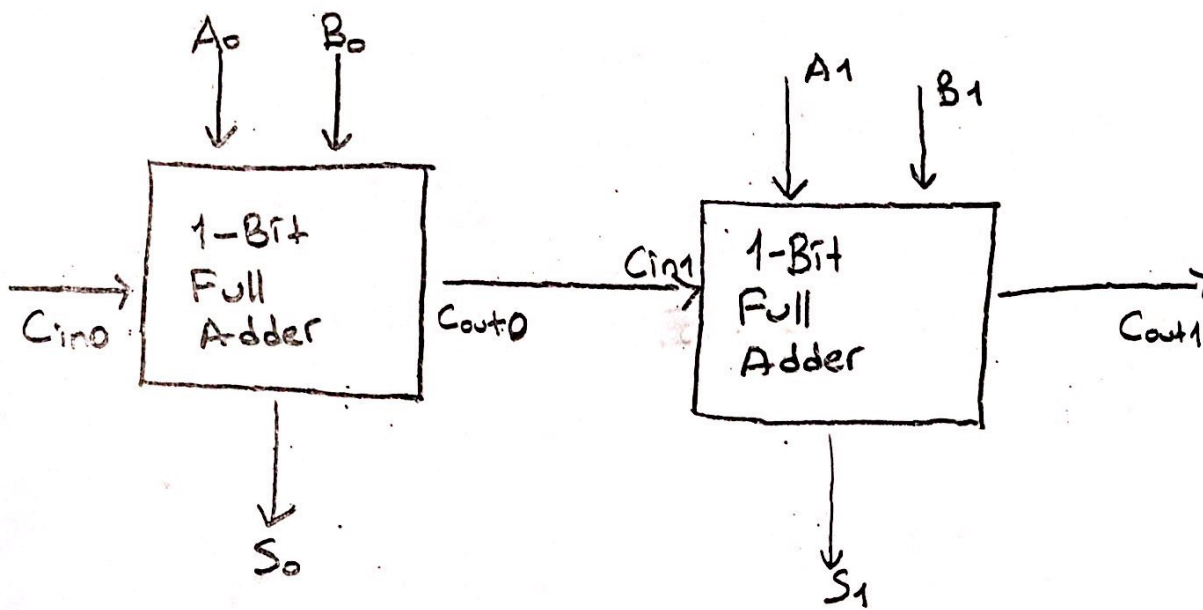


~ 2-Bit Full Adder ~



IC List

One 7486 Quad 2-Input XOR Gate
One 7408 Quad 2-Input AND Gate
One 7432 Quad 2-Input OR Gate

7486

GND-7

Vcc-14

7408

GND-7

Vcc-14

7432

GND-7

Vcc-14